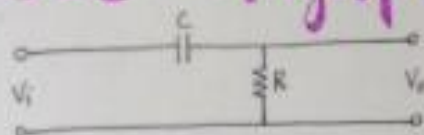


FILTERS

A CIRCUIT WHOSE OUTPUT VOLTAGE AMPLITUDE VARIES AS A FUNCTION OF FREQUENCY COMPARED TO THE INPUT VOLTAGE AMPLITUDE.

RL - highpass



* RC HIGH-PASS FILTER

→ The above circuit is just a V divider.
→ But one of the impedances vary w/ frequency. ∴ V_o must also vary w/ frequency.

$$\rightarrow V_o = V_i \cdot \frac{R}{R + 1/j\omega C}$$

$$= \frac{V_i \omega RC}{j\omega RC + 1}$$

→ How does the V_o amplitude of w/ V_i amplitude as f changes?

$$\rightarrow H(j\omega) = V_o/V_i \text{ (frequency response)}$$

$$= \frac{j\omega RC}{j\omega RC + 1}$$


→ At the f extremes:

$\omega \rightarrow 0$: transfer fn $\rightarrow 0$. At low f , circuit behaves like DC.

$\omega \rightarrow \infty$: transfer fn $\rightarrow 1$.

→ Filter w/ 1 storage element: 1st order filter.

* TRANSFER FUNCTION GRAPH

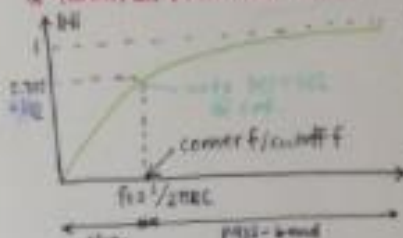


→ cut-off f :
 f_c @ which we have $\frac{1}{2}$ of possible power.
→ ∴ for $f < f_c$, filter passes < 50% power.

→ for $f > f_c$, filter passes > 50% power.
∴ HIGH PASS FILTER.

→ f_c : $\omega_c = 1/RC$

$$\therefore H(j\omega) = V_o/V_i = \frac{j\omega RC}{\sqrt{1 + (\omega RC)^2}}$$

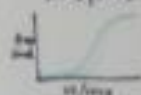→ Plotting ω/ω_c in log-scale, we will observe the response of circuit @ any f rel. to f_c .



→ We approximate by a Bode plot.
→ It's approximate by a Bode plot.
→ It's approximate by a Bode plot.

RC LOWPASS

* RC LOW-PASS FILTER

is Capacitor & resistor A.





$$\rightarrow V_o = V_i \cdot \frac{1}{j\omega RC + 1}$$

$$\therefore H(j\omega) = \frac{1}{j\omega RC + 1}$$


$$\rightarrow |H(j\omega)| = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

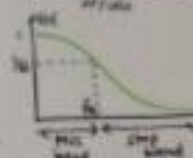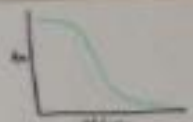→ Note: larger f = smaller A vice versa. ∴ low f passed thru.



BAND PASS FILTER


* BAND PASS FILTER

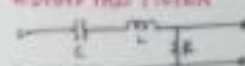

→ 2 in-series el.
→ 1st order filter.

$$\rightarrow V_o = V_i \cdot \frac{j\omega L}{j\omega L + R + 1/j\omega C} \quad \therefore H(j\omega) = \frac{j\omega L}{j\omega L + R + 1/j\omega C}$$

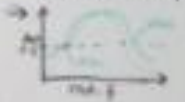→ At $\omega = 0$, impedance of C is large. ∴ no I.
At $\omega = \infty$, impedance of L is large. ∴ no I.



→ Basically a series RLC circuit, minus some.
→ $Z = \sqrt{R^2 + (\omega L - 1/\omega C)^2}$
→ $I = V/R$ @ $\omega_0 = 1/\sqrt{LC}$.

→ BPF has 2 f_c : $\omega_{c1} = 1/RC$ & $\omega_{c2} = R/L$

→ Bandwidth $B = \omega_2 - \omega_1$
→ ω_0 midway b/w 2 f_c 's.

* BPF & CUT OFF F

→ 50% P_{max} @ f_c ; Also, $I^2 R = \frac{1}{2} I_0^2 R$

$$\rightarrow I = I_0/\sqrt{2} = V/\sqrt{2}Z$$


$$\rightarrow I = V/\sqrt{2} = \frac{V}{\sqrt{R^2 + (\omega L - 1/\omega C)^2}}$$

→ For $\omega < \omega_0$, $X_L < X_C$; $\omega > \omega_0$, $X_L > X_C$

@ f_c ,
→ $R^2 = \sqrt{R^2 + (\omega L - 1/\omega C)^2}$ OR
→ $R^2 = \sqrt{R^2 + (\omega L - 1/\omega C)^2}$
→ $\therefore R^2 = R^2 + (\omega L - 1/\omega C)^2$
→ $\therefore 0 = (\omega L - 1/\omega C)^2$
→ $\therefore \omega = 1/\sqrt{LC}$

RL-FILTERS


* HIGH PASS

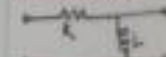

$$H(j\omega) = j\omega L / j\omega L + R$$

$$\omega_c = R/L$$

* LOW PASS

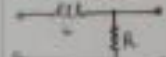

$$H(j\omega) = R / j\omega L + R$$

$$\omega_c = R/L$$

* CROSS OVER FILTERS:

→ Filters often used in audio systems w/ 2 or more loudspeakers.

